

Implement AWE

Name: Mohammed AL Shuaili

Date: 20/1/2025

AWE involves 4 main steps:

1. Form a state – space representation
2. Form the moments
3. Find the poles of the system
4. Find the residues

And then form the impulse response as:

$$h(t) = k_0\delta(t) + k_1e^{p_1t} + \dots + k_ne^{p_nt}$$

(1)

The following code implements AWE with first and second approximation:

```
1. clear all
2. clc
3. A = [-2 1 0 0; 1 -2 1 0; 0 1 -2 1; 0 0 1 -1];
4. B = [1; 0; 0; 0];
5. C = [1; 0; 0; 0];
6. q = length(B);
7. moments = zeros(1, 2*q-1);
8. for i=1:length(moments)
9.     moments(i) = -1*transpose(C)*A^-i*B;
10. end
11. %for first order approximation (Case 1)
12. b = -moments(2)/moments(1);
13. %the poles
14. p = -1/b;
15. % residues
16. k=-moments(1)*p;
17. %t = 0:0.01:0.5
18. %hence
19. ht1 = k*exp(p*t);
20. %Case 2
21. m2 = [moments(1),moments(2);moments(2),moments(3)];
22. m2_2 = -1*[moments(3);moments(4)];
23. b_case2 = inv(m2)*m2_2;
24. p_case2 = roots([b_case2(1),b_case2(2),1]);
25. %residues
26. V = [1 1 ; 1/p_case2(1) 1/p_case2(2)];
27. A_case2 = [1/p_case2(1) 0; 0 1/p_case2(2)];
28. k_case2 = -1* inv(A_case2) * inv(V) * [moments(1);moments(2)];
29. % hence the final expersion is
30. ht_case2 = k_case2(1)*exp(p_case2(1)*t)+k_case2(2)*exp(p_case2(2)*t);
31.
```

This code takes the input as matrices A, B and C. For example let:

$$A = \begin{bmatrix} -2 & 1 & 0 & 0 \\ 1 & -2 & 1 & 0 \\ 0 & 1 & -2 & 1 \\ 0 & 0 & 1 & -1 \end{bmatrix}, B = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix} \text{ and } C = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

(2)

First one must find the moments as follows:

$$m_i = -C^T A^{-i+1} B$$

Where (i) goes from 0 to 2q-1 and q is the order of the transfer function associated with the equation or the state space.

In example 1 we can find that,

$$m_0 = 1, m_1 = -4, m_2 = 30, m_3 = -246, m_4 = 2037, m_5 = -16886, m_6 = 140000$$

Next, find b (coefficients of s in the Laplace expression) as follows:

$$\begin{bmatrix} m_0 & \dots & m_{q-1} \\ m_1 & & m_q \\ \vdots & & \vdots \\ m_{q-1} & & m_{2q-1} \end{bmatrix} \begin{bmatrix} b_q \\ b_{q-1} \\ \vdots \\ b_1 \end{bmatrix} = - \begin{bmatrix} m_q \\ m_{q+1} \\ \vdots \\ m_{2q-1} \end{bmatrix}$$

Then solve for B(s)=0 to obtain the poles of the system where:

$$b_q s^q + b_{q-1} s^{q-1} \dots + b_1 s + 1 = 0$$

Next, finding the residues as:

$$k = -\Lambda V^{-1} \begin{bmatrix} m_0 \\ \vdots \\ m_{q-1} \end{bmatrix}$$

So, back to example 1, since q = 4, we can find that for a first order approximation:

$$b_1 = 4, \text{ Thus, } p = -0.25 \text{ and } k = 0.5$$


Hence using the general expression in (1) we obtain,

$$h(t) = 0.25e^{-0.25t}$$

in the same manner we can then find second, third and fourth order approximations.

- RLC ladder implementation

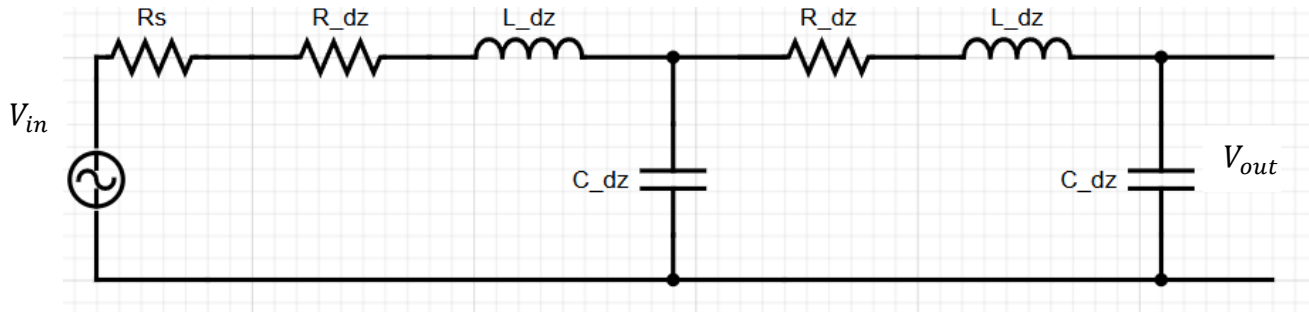Now, consider the open voltage RLC ladder for the transmission line with N=2 as follows:



From the circuit, we can say that:

$$v_{in} = (R_s + R_{dz})i_1 + L_{dz} \frac{di_1}{dt} + v_1 \quad (3)$$

$$v_1 = R_{dz}i_2 + L_{dz} \frac{di_2}{dt} + v_{out}$$

$$i_1 - i_2 = C \frac{dv_1}{dt}$$

$$i_2 = C \frac{dv_o}{dt}$$

So,

$$v_{in} = (R_s + R_{dz})i_1 + L_{dz} \frac{di_1}{dt} + R_{dz}i_2 + L_{dz} \frac{di_2}{dt} + v_{out}$$

Let,

$$x_1 = i_1, \quad x_2 = v_1, \quad x_3 = i_2 \quad \text{and} \quad x_4 = v_o$$

$$x = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ v_1 \\ i_2 \\ v_o \end{bmatrix}$$

Rewriting the equations,

$$\frac{di_1}{dt} = -\frac{(R_s + R_{dz})}{L_{dz}} i_1 - \frac{v_1}{L_{dz}} + \frac{v_{in}}{L_{dz}}$$

$$\frac{di_2}{dt} = \frac{-R_{dz}i_2}{L_{dz}} - \frac{v_{out}}{L_{dz}} + v_1$$

$$\frac{dv_1}{dt} = \frac{1}{C} (i_1 - i_2)$$

$$\frac{dv_o}{dt} = \frac{1}{C} i_2$$

Now, express them in terms of the state variables.

1. For $\frac{dx_1}{dt}$:

$$\frac{dx_1}{dt} = -\frac{(R_s + R_{dz})}{L_{dz}} x_1 - \frac{x_2}{L_{dz}} + \frac{v_{in}}{L_{dz}}$$

2. For $\frac{dx_2}{dt}$:

$$\frac{dx_2}{dt} = \frac{1}{C}(x_1 - x_3)$$

3. For $\frac{dx_3}{dt}$:

$$\frac{dx_3}{dt} = \frac{-R_{dz}x_3}{L_{dz}} - \frac{x_4}{L_{dz}} + x_2$$

4. For $\frac{dx_4}{dt}$:

$$\frac{dx_4}{dt} = \frac{1}{C} x_3$$

Step 2: Write in State-Space Form

$$\dot{x} = Ax + Bu, \quad y = Cx + Du$$

Where:

$$x = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{bmatrix} = \begin{bmatrix} i_1 \\ v_1 \\ i_2 \\ v_o \end{bmatrix}, \quad u = v_{in}, \quad y = v_{out}$$

Matrix A:

$$A = \begin{bmatrix} \frac{-R_s + R_{dz}}{L_{dz}} & -\frac{1}{L_{dz}} & 0 & 0 \\ \frac{1}{C} & 0 & -\frac{1}{C} & 0 \\ 0 & \frac{1}{L_{dz}} & -\frac{R_{dz}}{L_{dz}} & -\frac{1}{L_{dz}} \\ 0 & 0 & \frac{1}{C} & 0 \end{bmatrix}$$

Matrix B:


$$B = \begin{bmatrix} \frac{1}{L_{dz}} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Matrix C:

$$C = [0 \quad 0 \quad 0 \quad 1]$$

Now, let's implement AWE with these on MATLAB and compare it to ode45 for validation.

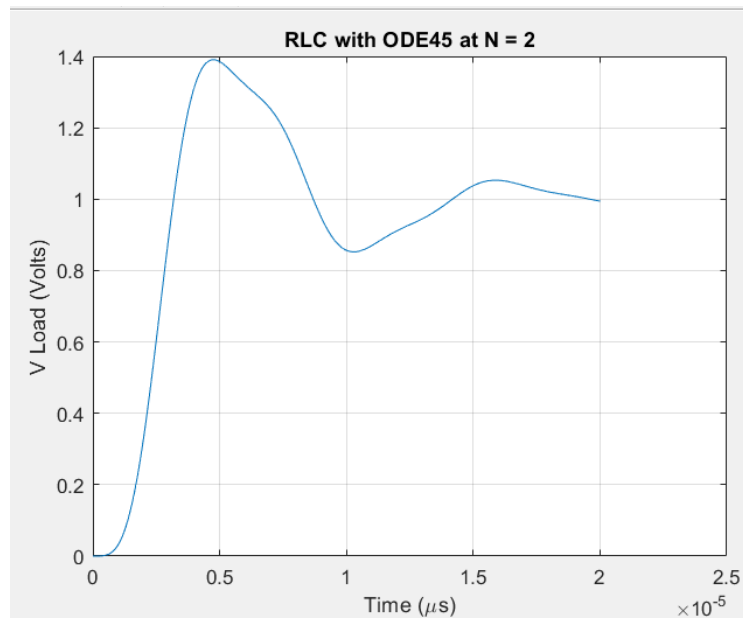This is the expected output (from ode45).



The cod:

```



1. clear all
2. clc
3. l = 400;
4. N = 2;
5. dz = 1/N;
6. R = 0.1*dz;
7. L = 2.5e-7*dz;
8. C = 1e-10*dz;
9. Rs = 0;
10. Vs = 30; % this is u
11. A = [-(Rs+R)/L, -1/L, 0, 0;
12.      1/C, 0, -1/C, 0;
13.      0, 1/L, -R/L, -1/L;
14.      0, 0, 1/C, 0];
15. B = [1/L;0;0;0].*Vs;
16. C = [0;0;0;1];
17. q = length(B);
18. moments = zeros(1,2*q-1);
19. for i=1:length(moments)
20.     moments(i) = -1*transpose(C)*A^-i*B;
21. end
22. %for first order approximation (Case 1)
23. b = -moments(2)/moments(1);
24. %the poles
25. p = -1/b;
26. % residues
27. k=-moments(1)*p;
28. %t =
29. %hense
30. t = 0:1e-10:20e-6;
31. ht1 = k*exp(p*t);
32. %Case 2
33. m2 = [moments(1),moments(2);moments(2),moments(3)];

```

```

34. m2_2 = -1*[moments(3);moments(4)];
35. b_case2 = m2^-1*m2_2;
36. p_case2 = roots([b_case2(1),b_case2(2),1]);
37. %residues
38. V = [1 1 ;1/p_case2(1) 1/p_case2(2)];
39. A_case2 = [1/p_case2(1) 0;0 1/p_case2(2)];
40. k_case2 = -1* inv(A_case2) * inv(V) * [moments(1);moments(2)];
41. % hence the final expersion is
42. ht_case2 = k_case2(1)*exp(p_case2(1)*t)+k_case2(2)*exp(p_case2(2)*t);
43. figure(1)
44. plot(t,ht1);
45. grid on
46. xlabel('Time (\mus)');
47. ylabel('V Load (Volts)');
48. title(['RLC with AWE first order at N = ',num2str(N)]);
49. figure(2)
50. plot(t,ht_case2);
51. grid on
52. xlabel('Time (\mus)');
53. ylabel('V Load (Volts)');
54. title(['RLC with AWE second order at N = ',num2str(N)]);
55.

```

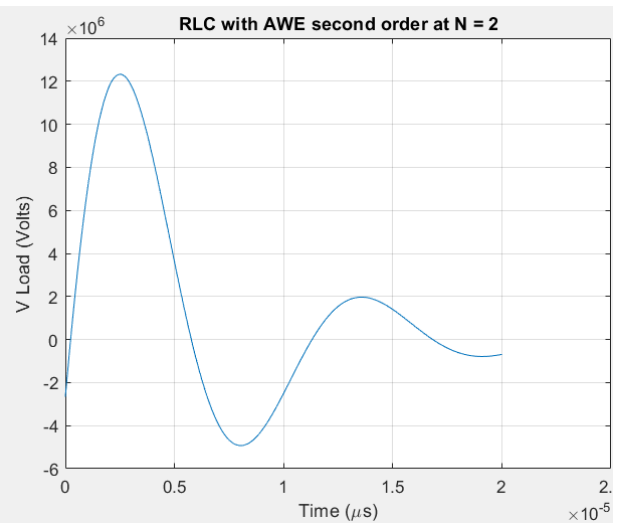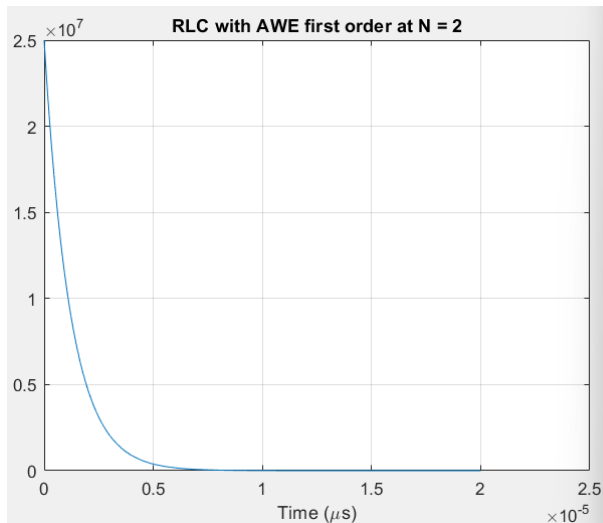

Looking at the first and second order approximations, they don't match the expected outputs from ode45.

Let's investigate the third order approximation.

$$\begin{bmatrix} m_0 & m_1 & m_2 \\ m_1 & m_2 & m_3 \\ m_2 & m_3 & m_4 \end{bmatrix} \begin{bmatrix} b_3 \\ b_2 \\ b_1 \end{bmatrix} = - \begin{bmatrix} m_3 \\ m_4 \\ m_5 \end{bmatrix}$$

Using the matrices above, the moments can be found as follows:

$$m_0 = 1, m_1 = -1.2e - 6, m_2 = -1.72e - 12, m_3 = 5.05e - 18, m_4 = -6.72e - 25, m_5 = -1.2595e - 29$$


Thus,

$$b_3 = -1.3270e - 18, b_2 = -3.1441e - 12, b_1 = -1.5175e - 6$$

And ,


$$V = \begin{bmatrix} \frac{1}{p_1} & \frac{1}{p_2} & \frac{1}{p_3} \\ \frac{1}{p_1^2} & \frac{1}{p_2^2} & \frac{1}{p_3^2} \end{bmatrix}, \quad \Lambda = \begin{bmatrix} \frac{1}{p_1} & 0 & 0 \\ 0 & \frac{1}{p_2} & 0 \\ 0 & 0 & \frac{1}{p_3} \end{bmatrix}, \quad k = \begin{bmatrix} k_1 \\ k_2 \\ k_3 \end{bmatrix}$$

Hence,

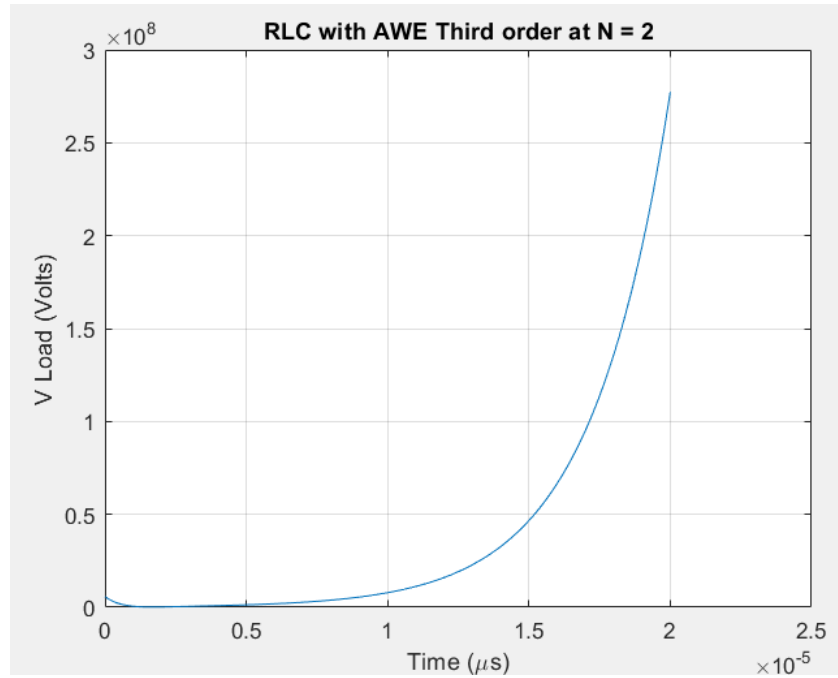

This is still not close to the expected result as in ode45.

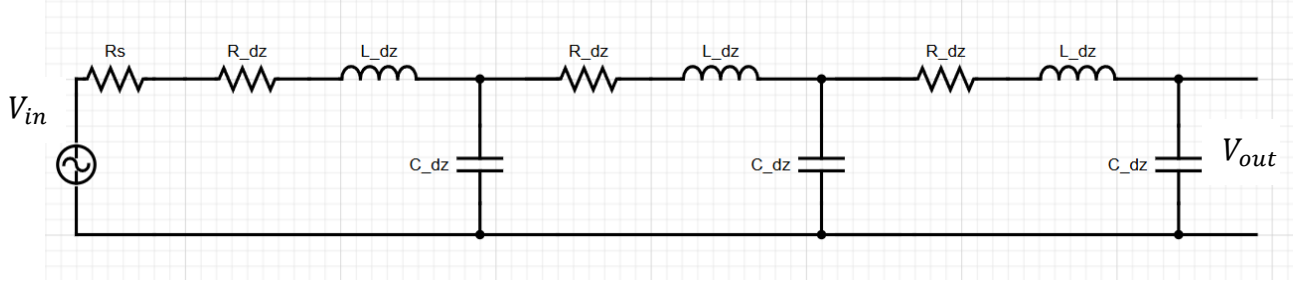Now, Let's consider the following circuit (RLC ladder with $N = 3$ and open voltage) to find a pattern where we can link the number of sections to the state space model:



$$v_{in} = (R_s + R_{dz})i_1 + L_{dz} \frac{di_1}{dt} + v_1$$

$$v_1 = R_{dz}i_2 + L_{dz} \frac{di_2}{dt} + v_2$$

$$v_2 = R_{dz}i_3 + L_{dz} \frac{di_3}{dt} + v_{out}$$

$$i_1 - i_2 = C \frac{dv_1}{dt}$$

$$i_2 - i_3 = C \frac{dv_2}{dt}$$

$$i_3 = C \frac{dv_o}{dt}$$

$$v_{in} = (R_s + R_{dz})i_1 + L_{dz} \frac{di_1}{dt} + R_{dz}i_2 + L_{dz} \frac{di_2}{dt} + R_{dz}i_3 + L_{dz} \frac{di_3}{dt} + v_{out}$$

Let,

$$x = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \\ x_6 \end{bmatrix} = \begin{bmatrix} i_1 \\ v_1 \\ i_2 \\ v_2 \\ i_3 \\ v_o \end{bmatrix}, \quad u = v_{in}, \quad y = v_{out}$$

So, each section of the transmission line contributes two states to the state-space model:

What to do next (in the meantime):

1. Find what causing the issue for the AWE

Y and S parameters:

Y-parameters, or admittance parameters, characterize the electrical behavior of transmission lines in network analysis by relating port voltages and currents. They are used for modeling high-frequency circuits, especially in microwave design, as they describe how a network admits current in response to voltage.

For a two-port network:

- **Y₁₁**: Input admittance at port 1 (port 2 shorted).
- **Y₁₂**: Reverse admittance from port 2 to port 1.
- **Y₂₁**: Forward admittance from port 1 to port 2.
- **Y₂₂**: Output admittance at port 2 (port 1 shorted).

These parameters are key for understanding transmission line interactions with other components [1].

[1] A. Arrais and R. Levy, "Direct Y-Parameter Estimation of Microwave Structures Using TLM Simulation and Prony's Method," *ResearchGate*, [Online]. Available: https://www.researchgate.net/publication/230844927_Direct_Y-parameter_estimation_of_microwave_structures_using_TLM_simulation_and_Prony's_method. [Accessed: Jan. 25, 2025].

Further research can be done, at this time the IEEE website is down.

IEEE Xplore is temporarily unavailable

We are working to restore service as soon as possible. Please try again later or email questions to onlinesupport@ieee.org. We apologize for the inconvenience and appreciate your patience.