

The Y-parameters of the transmission line are

$$\begin{bmatrix} I_S \\ -I_R \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_S \\ V_R \end{bmatrix}$$

Suppose that these are determined from experiment.

Approximate each with a rational function

$$Y_{ij} = \frac{a_{nij}s^{n-1} + \dots + a_{0ij}}{s^n + \dots + b_{0ij}}$$

Consider the open-circuit case

$$I_R = 0$$

$$\begin{aligned} \frac{V_R}{V_S} &= -\frac{Y_{21}}{Y_{22}} = f\left(\frac{a_{n21}s^{n-1} + \dots + a_{021}}{s^n + \dots + b_{021}}, \frac{a_{n22}s^{n-1} + \dots + a_{022}}{s^n + \dots + b_{022}}\right) = -\frac{\frac{a_{n21}s^{n-1} + \dots + a_{021}}{s^n + \dots + b_{021}}}{\frac{a_{n22}s^{n-1} + \dots + a_{022}}{s^n + \dots + b_{022}}} \\ &= \frac{f_{n-1}s^{n-1} + \dots + f_0}{s^n + g_{n-1}s^{n-1} + \dots + g_0} \end{aligned}$$

Convert this function to a state space.

This is done as described in systems notes.

Proceed to with AWE to get time domain model.